



NCF-003-11152004 Seat No. _____

M. Sc. (ELE) (Sem. II) (CBCS) Examination
April / May - 2017

Advanced Digital Electronics : Paper - VIII

Faculty Code : 003

Subject Code : 11152004

Time : $2\frac{1}{2}$ Hours]

[Total Marks : 70

1 Answer the following questions in brief : (any seven) **14**

- (1) Explain working of multiplexer as parallel to serial converter.
- (2) Mention the steps to implement combinational logic circuit.
- (3) Draw the circuit diagram and explain working of half adder in brief.
- (4) Compare fixed logic to programmable logic.
- (5) Explain in brief synchronous and asynchronous inputs to FlipFlops.
- (6) Explain modulus of counter.
- (7) Explain working of RS Flip-Flop as key de-bouncer.
- (8) Compare asynchronous counter with synchronous counter.
- (9) Enlist all registers available with 8085.
- (10) Classify instructions of 8085 in various categories.

2 Attempt any two of the following questions : (Each 7 Marks) **14**

- (1) With help of necessary diagram and derivations explain working of look ahead carry propagator.
- (2) Give a detailed account on Complex Programmable Logic Devices (CPLD) architecture.
- (3) Enlist various types of shift registers. Explain working of any two types of shift registers with help of necessary diagrams.

- 3** Answer the following questions :
- (1) Describe Programmable Logic Array (PLA) architecture. **5**
 - (2) Design a mod-5 synchronous counter and explain its working with help of neat diagram. **5**
 - (3) Write a program to find the largest number of the 20 numbers stored at 2000H onwards. Store the same in Register B. **4**

OR

- 3** Answer the following questions :
- (1) With neat diagrams explain working of half and full subtractor. **5**
 - (2) With neat diagram explain the working of a 4-bit ring counter. **5**
 - (3) Write a detailed note on X Flip-Flop. **4**
- 4** Answer the following questions :
- (1) What is multiplexer? With help of necessary circuit diagram explain working of a 4 to 1 multiplexer. **5**
 - (2) Write a note on astable multivibrator. **5**
 - (3) Explain working of 3-bit binary asynchronous counter with help of neat diagram. **4**
- 5** Answer any two of the following questions. (Each 7 Marks) **14**
- (1) What is a magnitude comparator? With neat circuit explain its working.
 - (2) Enlist and explain various timing parameters of Flip-Flop.
 - (3) With help of neat diagrams explain working of 3-bit binary asynchronous up-down counter.
 - (4) Draw and explain the functional block diagram of 8085.